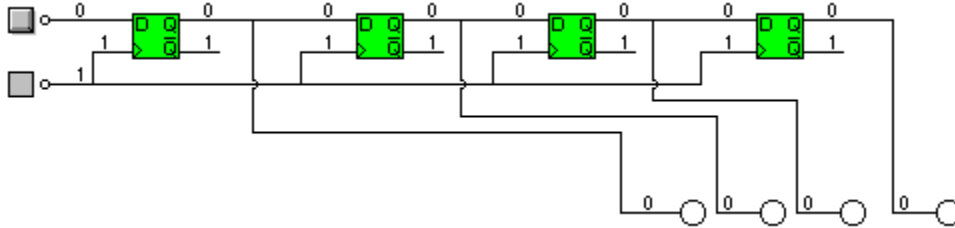



Shift Registers

Build the following shift register circuits in Crocodile Physics. For each one identify the type of shift register it represents by filling in the blank above it. Then describe the function of all inputs (switches) and outputs (LEDs) by labeling them on this page.

1. _____



2. _____

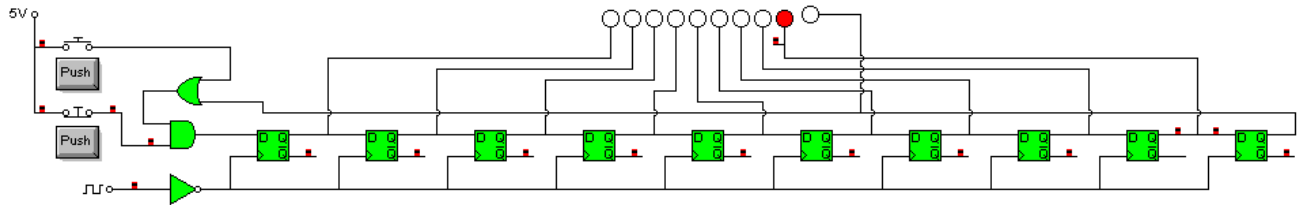

3. _____

